Question 1(a) [3 marks]

State importance of scaling

Answer:

Scaling is crucial for advancing semiconductor technology and improving device performance.

Scaling Benefits	Description
Device Size	Reduces transistor dimensions for higher density
Speed	Faster switching due to shorter channel length
Power	Lower power consumption per operation
Cost	More chips per wafer, reducing cost per function

• Technology advancement: Enables Moore's Law continuation

• Performance boost: Higher frequency operation possible

• Market competitiveness: Smaller, faster, cheaper products

Mnemonic: "Small Devices Speed Progress Cheaply"

Question 1(b) [4 marks]

Compare Planar MOSFET and FINFET

Answer:

FinFET technology addresses limitations of planar MOSFET at smaller nodes.

Parameter	Planar MOSFET	FinFET
Structure	2D flat channel	3D fin-shaped channel
Gate Control	Single gate	Tri-gate/multi-gate
Short Channel Effects	High at small nodes	Significantly reduced
Leakage Current	Higher subthreshold leakage	Much lower leakage

• Scalability: FinFET enables sub-22nm technology nodes

• **Power efficiency**: FinFET offers better power-performance ratio

• Manufacturing: FinFET requires more complex fabrication

Mnemonic: "Fins Control Current Better Than Flat"


Question 1(c) [7 marks]

Draw and Explain VDS-ID AND VGS-ID characteristics of N channel MOSFET

Answer:

N-channel MOSFET characteristics show device behavior in different operating regions.

Diagram:

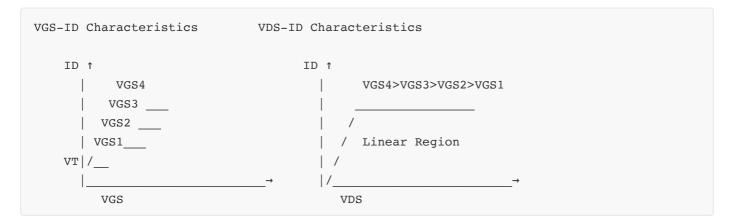

Region	Condition	Current Equation
Cutoff	VGS < VT	ID = 0
Linear	VDS < (VGS-VT)	ID ∝ VDS
Saturation	VDS ≥ (VGS-VT)	ID ∝ (VGS-VT)²

• Threshold voltage (VT): Minimum VGS for conduction

• **Transconductance**: Slope of VGS-ID curve in saturation

• Output resistance: Inverse slope in saturation region

Mnemonic: "Threshold Gates Linear Saturation"


Question 1(c OR) [7 marks]

Explain different condition of MOS under external bias

Answer

External bias creates different charge distributions affecting MOS capacitor behavior.

Diagram:

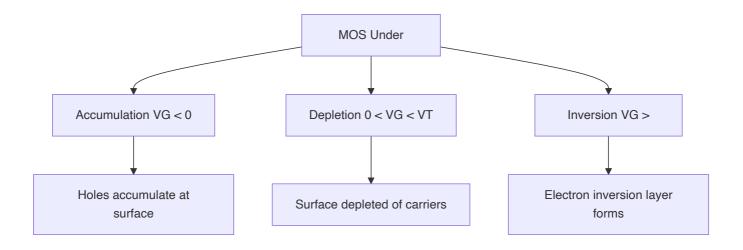

Bias Condition	Surface State	Capacitance
Accumulation	Majority carriers at surface	High (Cox)
Depletion	No mobile carriers	Medium
Inversion	Minority carriers form channel	High (Cox)

- Flat band voltage: No charge separation exists
- Energy band bending: Determines carrier distribution
- **Surface potential**: Controls inversion layer formation

Mnemonic: "Accumulate, Deplete, then Invert"


Question 2(a) [3 marks]

Draw voltage transfer characteristic of ideal inverter

Answer:

Ideal inverter provides sharp transition between logic levels with infinite gain.

Diagram:

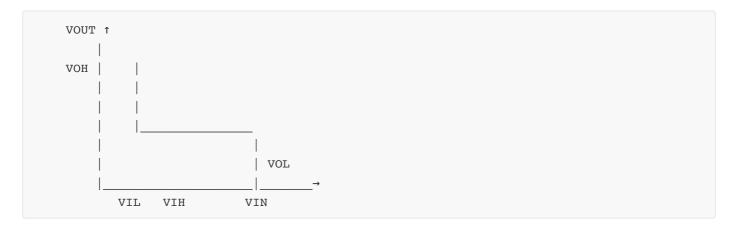

• Sharp transition: Infinite slope at switching point

• Noise margins: NMH = VOH - VIH, NML = VIL - VOL

• Perfect logic levels: VOH = VDD, VOL = 0V

Mnemonic: "Sharp Switch, Perfect Levels"

Question 2(b) [4 marks]

Explain noise immunity and noise margin

Answer:

Noise immunity measures circuit's ability to reject unwanted signal variations.

Parameter	Definition	Formula
NMH	High-level noise margin	VOH - VIH
NML	Low-level noise margin	VIL - VOL
Noise Immunity	Ability to reject noise	Min(NMH, NML)

• Logic threshold levels: VIH (input high), VIL (input low)

• Output levels: VOH (output high), VOL (output low)

• Better immunity: Larger noise margins provide better protection

• **Design goal**: Maximize noise margins for robust operation

Mnemonic: "Margins Protect Against Noise"

Question 2(c) [7 marks]


Describe inverter circuit with saturated and linear depletion load nMOS inverter

Answer:

Depletion load nMOS inverters use depletion transistor as active load resistor.

Diagram:



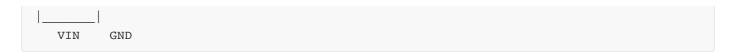

Load Type	Gate Connection	Operation
Saturated Load	VG = VD	Always in saturation
Linear Load	VG = VDD	Can operate in linear region

• **Depletion device**: Conducts with VGS = 0, acts as current source

• Load line analysis: Determines operating point intersection

• Power consumption: Always conducting, higher static power

• Switching speed: Faster pull-down than pull-up

Mnemonic: "Depletion Loads Drive Outputs"

Question 2(a OR) [3 marks]

Draw and explain enhancement load inverter

Answer:

Enhancement load inverter uses enhancement MOSFET as load with special biasing.

Diagram:

• Bootstrap connection: Gate connected to drain for load

• Limited output high: VOUT(max) = VDD - VT

• Threshold loss: Enhancement load causes voltage drop

Mnemonic: "Enhancement Loses Threshold"

Question 2(b OR) [4 marks]

List the advantages of CMOS inverter

Answer:

CMOS technology offers superior performance compared to NMOS inverters.

Advantage	Benefit
Zero static power	No current path in steady state
Rail-to-rail output	Full VDD and 0V output levels
High noise immunity	Large noise margins
Symmetric switching	Equal rise and fall times

- Power efficiency: Only dynamic power during switching
- Scalability: Works well at all technology nodes
- Fan-out capability: Can drive multiple inputs
- **Temperature stability**: Performance less sensitive to temperature

Mnemonic: "CMOS Saves Power Perfectly"


Question 2(c OR) [7 marks]

Draw and Explain operating mode of region for CMOS Inverter

Answer:

CMOS inverter operation involves five distinct regions based on input voltage.

Diagram:

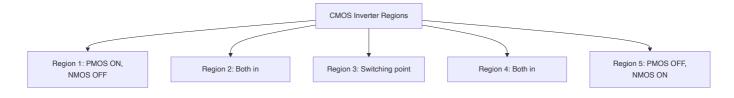

Region	NMOS State	PMOS State	Output
1	OFF	Linear	VOH ≈ VDD
2	Saturation	Saturation	Transition
3	Saturation	Saturation	VDD/2
4	Saturation	Saturation	Transition
5	Linear	OFF	VOL≈0V

• Switching threshold: VTC crosses VDD/2 at region 3

• Current flow: Only during transition regions 2,3,4

• Noise margins: Regions 1 and 5 provide immunity

• Gain: Maximum in region 3 (switching point)

Mnemonic: "Five Regions Control CMOS Switching"

Question 3(a) [3 marks]

Draw two input NOR gate using CMOS

Answer:

CMOS NOR gate implements De Morgan's law using complementary networks.

Diagram:



- **Pull-up network**: Series PMOS transistors (A AND B both low for high output)
- Pull-down network: Parallel NMOS transistors (A OR B high for low output)
- **Logic function**: Y = (A+B)' = A' · B'

Mnemonic: "Series PMOS, Parallel NMOS"


Question 3(b) [4 marks]

Implement Boolean function Z= [(A+B)C+DE]' using CMOS

Answer:

Complex CMOS logic uses AOI (AND-OR-Invert) structure for efficient implementation.

Diagram:

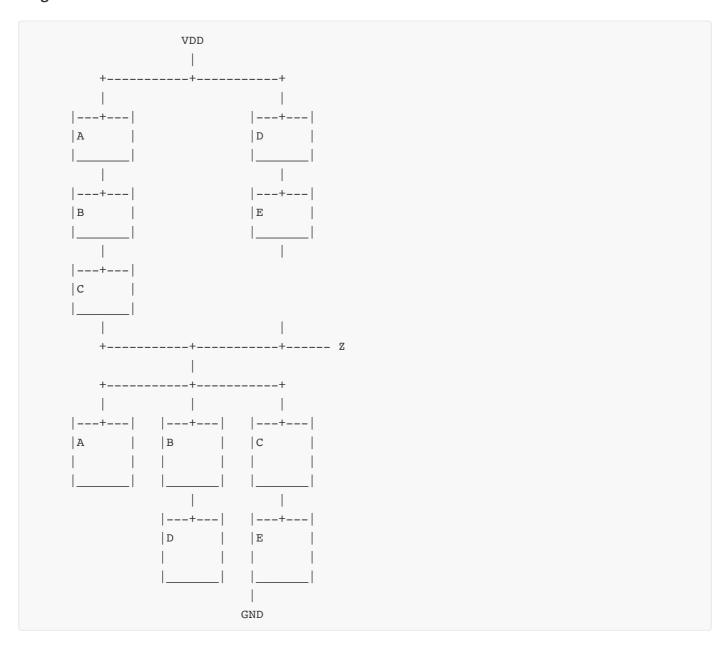

- **AOI structure**: Efficient single-stage implementation
- **Dual networks**: Complementary pull-up and pull-down
- Logic optimization: Fewer transistors than separate gates

Mnemonic: "AOI Inverts Complex Logic Efficiently"


Question 3(c) [7 marks]

Draw and explain CMOS NAND2 gate with the parasitic device capacitances

Answer:

Parasitic capacitances in CMOS gates affect switching speed and power consumption.

Diagram:

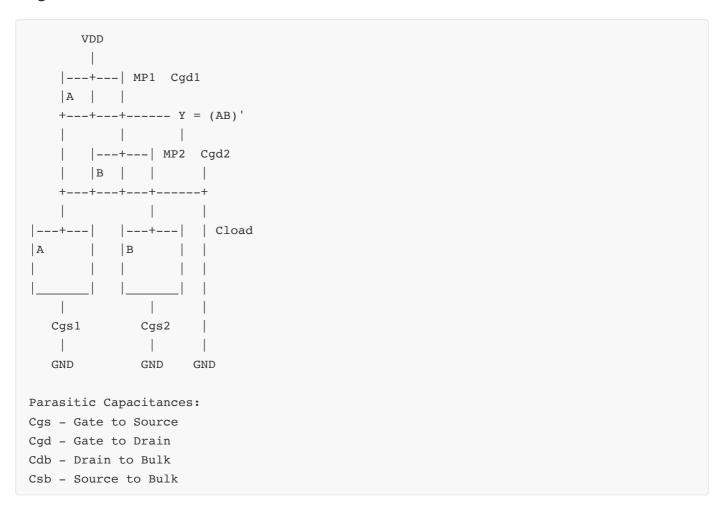

Capacitance	Location	Effect
Cgs	Gate-Source	Input capacitance
Cgd	Gate-Drain	Miller effect
Cdb	Drain-Bulk	Output loading
Csb	Source-Bulk	Source loading

- Switching delay: Parasitic capacitances slow transitions
- Power consumption: Charging/discharging parasitic caps
- Miller effect: Cgd creates feedback, slows switching
- Layout optimization: Minimize parasitic capacitances

Mnemonic: "Parasitics Slow Gates Down"


Question 3(a OR) [3 marks]

Draw and explain NOR based Clocked SR latch using CMOS

Answer:

Clocked SR latch uses NOR gates with clock enable for synchronous operation.

Diagram:

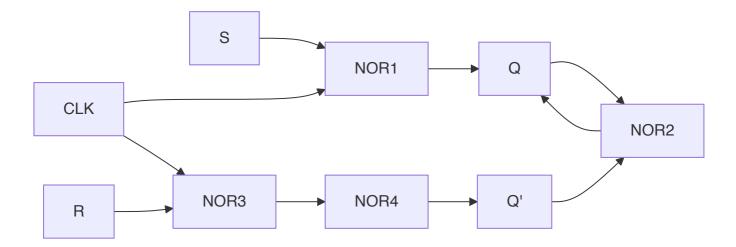

- Clock control: S and R effective only when CLK = 1
- Transparent mode: Output follows input when clock active
- Hold mode: Output maintains state when clock inactive
- Basic building block: Foundation for flip-flops

Mnemonic: "Clock Controls Transparent Latching"

Question 3(b OR) [4 marks]

Implement Boolean function Z=[AB+C(D+E)]' using CMOS

Answer:

This function implements inverted sum-of-products using AOI logic structure.

Logic Analysis:

- Original: Z = [AB + C(D+E)]'
- Expanded: Z = [AB + CD + CE]'
- Implementation: Three AND terms fed to NOR

Term	Inputs	Function
Term 1	А, В	AB
Term 2	C, D	CD
Term 3	C, E	CE
Output	All terms	(AB + CD + CE)'

• AOI implementation: Single stage, efficient design

• **Transistor count**: Fewer than separate gate implementation

• **Performance**: Fast switching, low power

Mnemonic: "Three AND Terms Feed One NOR"

Question 3(c OR) [7 marks]

Differentiate AOI and OAI Logic with example

Answer:

AOI and OAI are complementary logic families for efficient CMOS implementation.

Parameter	AOI (AND-OR-Invert)	OAI (OR-AND-Invert)
Structure	AND gates \rightarrow OR \rightarrow Invert	$OR \ gates \rightarrow AND \rightarrow Invert$
Function	(AB + CD +)'	((A+B)(C+D))'
PMOS Network	Series-parallel	Parallel-series
NMOS Network	Parallel-series	Series-parallel

AOI Example: Y = (AB + CD)'

```
PMOS: Series A-B in parallel with Series C-D
NMOS: Parallel A,B in series with Parallel C,D
```

OAI Example: Y = ((A+B)(C+D))'

```
PMOS: Parallel A,B in series with Parallel C,D
NMOS: Series A-B in parallel with Series C-D
```

• Design choice: Select based on Boolean function form

• Optimization: Minimizes transistor count and delay

• **Duality**: AOI and OAI are De Morgan duals

Mnemonic: "AOI ANDs then ORs, OAI ORs then ANDs"

Question 4(a) [3 marks]

Define: 1) Regularity 2) Modularity 3) Locality

Answer:

Design hierarchy principles essential for managing VLSI complexity and ensuring successful implementation.

Principle	Definition	Benefit
Regularity	Repeated use of similar structures	Easier layout, testing
Modularity	Breaking design into smaller blocks	Independent design, reuse
Locality	Interconnections mostly local	Reduced routing complexity

• **Design efficiency**: Principles reduce design time and effort

• Verification: Modular approach simplifies testing

• Scalability: Enables larger, more complex designs

Mnemonic: "Regular Modules Stay Local"


Question 4(b) [4 marks]

Implement SR latch (NAND gate) using CMOS inverter

Answer:

SR latch using NAND gates provides set-reset functionality with active-low inputs.

Diagram:

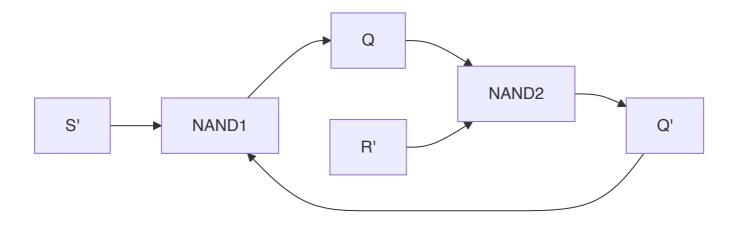

Truth Table:

S'	R'	Q	Q'	State
0	1	1	0	Set
1	0	0	1	Reset
1	1	Q	Q'	Hold
0	0	1	1	Invalid

• Cross-coupled structure: Provides memory function

• Active-low inputs: S' = 0 sets, R' = 0 resets

• Forbidden state: Both inputs low simultaneously

Mnemonic: "Cross-Coupled NANDS Remember State"

Question 4(c) [7 marks]

Explain VLSI design flow

Answer:

VLSI design flow follows systematic steps from specification to fabrication.



Level	Activities	Output	
System	Requirements analysis	Specifications	
Architecture	Block-level design	System architecture	
Logic	Boolean optimization	Gate netlist	
Circuit	Transistor sizing	Circuit netlist	
Physical	Layout, routing	GDSII file	

• **Design verification**: Each level requires validation

• Iteration: Feedback loops for optimization

CAD tools: Automation essential for complex designs

• Time-to-market: Efficient flow reduces design cycle

Mnemonic: "System Architects Love Circuit Physical Fabrication"


Question 4(a OR) [3 marks]

Draw and explain Y-chart

Answer:

Y-chart represents three design domains and their abstraction levels in VLSI design.

Diagram:

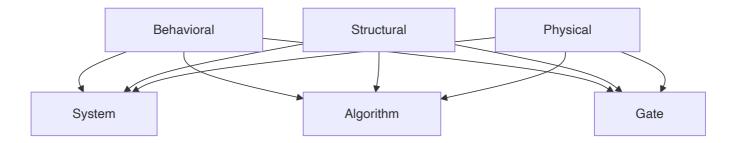

- Three domains: Behavioral (function), Structural (components), Physical (geometry)
- **Abstraction levels**: System \rightarrow Algorithm \rightarrow Gate \rightarrow Circuit \rightarrow Layout
- Design methodology: Move between domains at same abstraction level

Mnemonic: "Behavior, Structure, Physics at All Levels"


Question 4(b OR) [4 marks]

Implement clocked JK latch (NOR gate) using CMOS inverter

Answer:

JK latch eliminates forbidden state of SR latch with toggle capability.

Diagram:

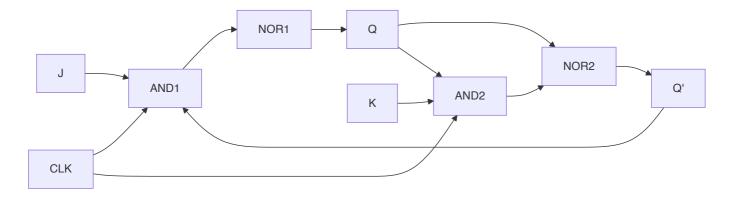

Truth Table:

J	K	Q(next)	Operation
0	0	Q	Hold
0	1	0	Reset
1	0	1	Set
1	1	Q'	Toggle

• Toggle mode: J=K=1 flips output state

• Clock enable: Active only when CLK=1

• Feedback: Uses current output to enable inputs

Mnemonic: "JK Toggles, No Forbidden State"

Question 4(c OR) [7 marks]

Explain the terms Lithography, Etching, Deposition, Oxidation, Ion implantation, Diffusion

Answer:

Semiconductor fabrication processes essential for creating integrated circuits.

Process	Purpose	Method
Lithography	Pattern transfer	UV exposure through masks
Etching	Material removal	Wet/dry chemical processes
Deposition	Layer addition	CVD, PVD, sputtering
Oxidation	Insulator growth	Thermal/plasma oxidation
Ion Implantation	Doping introduction	High-energy ion bombardment
Diffusion	Dopant distribution	High-temperature spreading

• **Pattern definition**: Lithography creates device features

• Selective removal: Etching removes unwanted material

• Layer building: Deposition adds required materials

• **Doping control**: Implantation and diffusion create junctions

• Quality control: Each step affects final device performance

Mnemonic: "Light Etches Deposited Oxides, Ions Diffuse"

Question 5(a) [3 marks]

Implement 2 input XNOR gate using Verilog

Answer:

XNOR gate produces high output when inputs are equal.

```
module xnor_gate(
    input a, b,
    output y
);
    assign y = ~(a ^ b);
endmodule
```

- **Logic function**: Y = (A ⊕ B)' = A'B' + AB
- Truth table: Output high when inputs match
- Applications: Equality comparator, parity checker

Mnemonic: "XNOR Equals Equal Inputs"

Question 5(b) [4 marks]

Implement Encoder (8:3) using CASE statement in Verilog

Answer:

Priority encoder converts 8-bit input to 3-bit binary output.

```
module encoder_8to3(
    input [7:0] in,
    output reg [2:0] out
);
    always @(*) begin
        case(in)
            8'b00000001: out = 3'b000;
            8'b00000010: out = 3'b001;
            8'b00000100: out = 3'b010;
            8'b00001000: out = 3'b011;
            8'b00010000: out = 3'b100;
            8'b001000000: out = 3'b101;
            8'b01000000: out = 3'b110;
            8'b10000000: out = 3'b111;
            default: out = 3'b000;
        endcase
    end
endmodule
```

- One-hot encoding: Only one input bit should be high
- **Priority structure**: Higher bits take precedence
- Default case: Handles invalid input combinations

Mnemonic: "One Hot Input, Binary Output"

Question 5(c) [7 marks]

Explain CASE statement in Verilog with suitable examples

Answer:

CASE statement provides multi-way branching based on expression value.

Syntax:

```
case (expression)
  value1: statement1;
  value2: statement2;
  default: default_statement;
endcase
```

Example 1 - 4:1 MUX:

```
module mux_4to1(
    input [1:0] sel,
    input [3:0] in,
    output reg out
);
    always @(*) begin
        case(sel)
        2'b00: out = in[0];
        2'b01: out = in[1];
        2'b10: out = in[2];
        2'b11: out = in[3];
        endcase
    end
endmodule
```

Example 2 - 7-Segment Decoder:

```
case(digit)
   4'h0: segments = 7'b11111110;
   4'h1: segments = 7'b0110000;
   4'h2: segments = 7'b1101101;
   default: segments = 7'b00000000;
endcase
```

Variant	Syntax	Use Case
case	case(expr)	Full matching
casex	casex(expr)	Don't care (X)
casez	casez(expr)	High-Z (Z)

- Combinational logic: Use always @(*) block
- Sequential logic: Use always @(posedge clk)

- Default case: Prevents latches in synthesis
- Parallel evaluation: All cases checked simultaneously

Mnemonic: "CASE Chooses Actions Systematically Everywhere"

Question 5(a OR) [3 marks]

Implement full subtractor using Verilog code

Answer:

Full subtractor performs binary subtraction with borrow input and output.

```
module full_subtractor(
   input a, b, bin,
   output diff, bout
);
   assign diff = a ^ b ^ bin;
   assign bout = (~a & b) | (~a & bin) | (b & bin);
endmodule
```

Truth Table:

Α	В	Bin	Diff	Bout
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
1	1	1	1	1

• Difference: XOR of all three inputs

• **Borrow**: Generated when A < (B + Bin)

Mnemonic: "Subtract Borrows When Insufficient"

Question 5(b OR) [4 marks]

Implement JK flipflop using Behavioural modeling style in Verilog

Answer:

JK flip-flop with toggle capability using behavioral modeling.

```
module jk_flipflop(
   input j, k, clk, reset,
   output reg q, qbar
);
```

```
always @(posedge clk or posedge reset) begin
       if(reset) begin
           q <= 1'b0;
           qbar <= 1'b1;
       end
       else begin
           case({j,k})
               2'b00: q <= q; // Hold
               2'b01: q <= 1'b0;
                                  // Reset
               2'b10: q <= 1'b1;
                                  // Set
               2'b11: q <= ~q; // Toggle
           endcase
           qbar <= ~q;
       end
   end
endmodule
```

• Behavioral style: Describes function, not structure

• Synchronous reset: Reset on clock edge

• Non-blocking assignment: Use <= in clocked always block

Mnemonic: "JK Behavior: Hold, Reset, Set, Toggle"

Question 5(c OR) [7 marks]

Explain different Verilog modeling style with examples

Answer:

Verilog provides three modeling styles for different abstraction levels.

Style	Abstraction	Description	Constructs
Behavioral	High	Describes function	always, if-else, case
Dataflow	Medium	Describes data movement	assign, operators
Structural	Low	Describes connections	module instantiation

1. Behavioral Modeling:

Describes what the circuit does, not how it's built.

```
// 4-bit counter
module counter(
   input clk, reset,
   output reg [3:0] count
);
   always @(posedge clk or posedge reset) begin
       if(reset)
            count <= 4'b0000;
       else
            count <= count + 1;
   end
endmodule</pre>
```

2. Dataflow Modeling:

Uses continuous assignments for combinational logic.

3. Structural Modeling:

Instantiates and connects lower-level modules.

```
// Full adder using half adders
module full_adder(
   input a, b, cin,
   output sum, cout
);
   wire s1, c1, c2;

   half_adder hal(.a(a), .b(b), .sum(s1), .carry(c1));
   half_adder ha2(.a(s1), .b(cin), .sum(sum), .carry(c2));

   assign cout = c1 | c2;
endmodule

module half_adder(
   input a, b,
   output sum, carry
);
   assign sum = a ^ b;
   assign carry = a & b;
```

endmodule

Comparison Table:

Aspect	Behavioral	Dataflow	Structural
Complexity	High-level	Medium-level	Low-level
Readability	Most readable	Moderate	Least readable
Synthesis	Tool dependent	Direct	Explicit
Debugging	Harder	Moderate	Easier
Reusability	High	Medium	High

Mixed Modeling Example:

```
module cpu_alu(
    input [7:0] a, b,
    input [2:0] opcode,
    input clk,
    output reg [7:0] result
);
    // Behavioral: Control logic
    always @(posedge clk) begin
        case(opcode)
            3'b000: result <= add_result;</pre>
            3'b001: result <= sub_result;</pre>
            3'b010: result <= and result;
            default: result <= 8'h00;
        endcase
    end
    // Dataflow: Arithmetic operations
    wire [7:0] add_result = a + b;
    wire [7:0] sub_result = a - b;
    wire [7:0] and result = a & b;
    // Structural: Could instantiate dedicated arithmetic units
endmodule
```

Design Guidelines:

- Behavioral: Use for complex control logic, state machines
- Dataflow: Use for simple combinational logic
- Structural: Use for hierarchical designs, IP integration
- Mixed approach: Combine styles for optimal design

Simulation vs Synthesis:

- **Behavioral**: May not synthesize as expected
- **Dataflow**: Direct hardware mapping
- **Structural**: Guaranteed synthesis match

Mnemonic: "Behavior Describes, Dataflow Assigns, Structure Connects"